
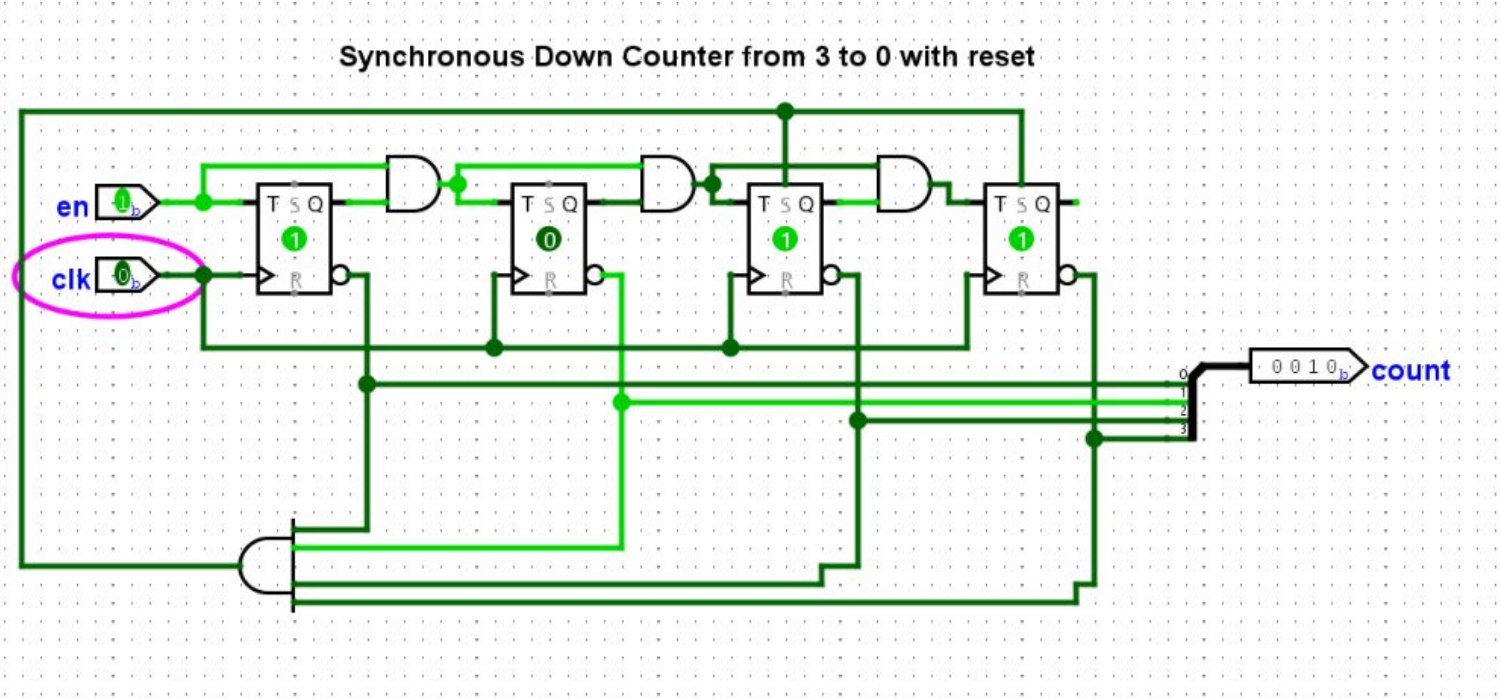
Lab 7- Traffic light


Eden Aklilu

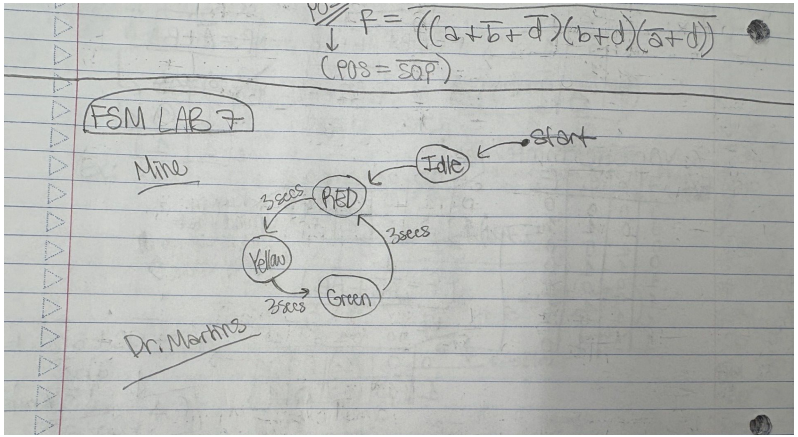3 ⇒ 0 by setting the flip flops to the complement of 3 (12),
Note: Q does opposite of not output below it




FSM Design



POS
$F = \overline{((a+\bar{b}+\bar{d})(b+d)(\bar{a}+d))}$
$(POS = \overline{SOP})$
FSM LAB 7
Mine
Idle
start
RED
3secs
Yellow
Green
Dr. Martins

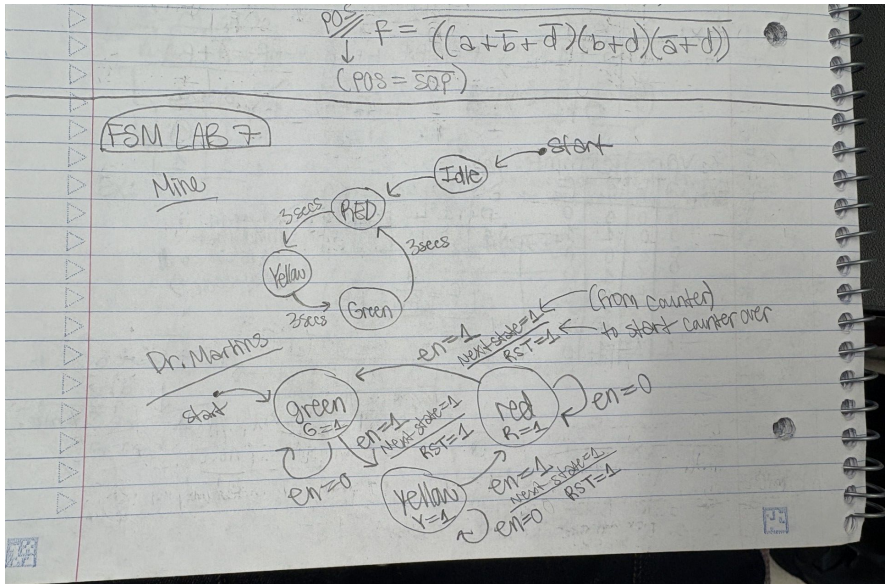
POS
$F = \overline{((a+\bar{b}+\bar{d})(b+d)(\bar{a}+d))}$
$(POS = \overline{SOP})$
FSM LAB 7
Mine
Idle
start
RED
3secs
Yellow
Green
Dr. Martins
start
green
G=1
red
R=1
yellow
Y=1
en=1
Next_state=1
RST=1
en=0
(from counter)
to start counter over

Truth table for multiplexer

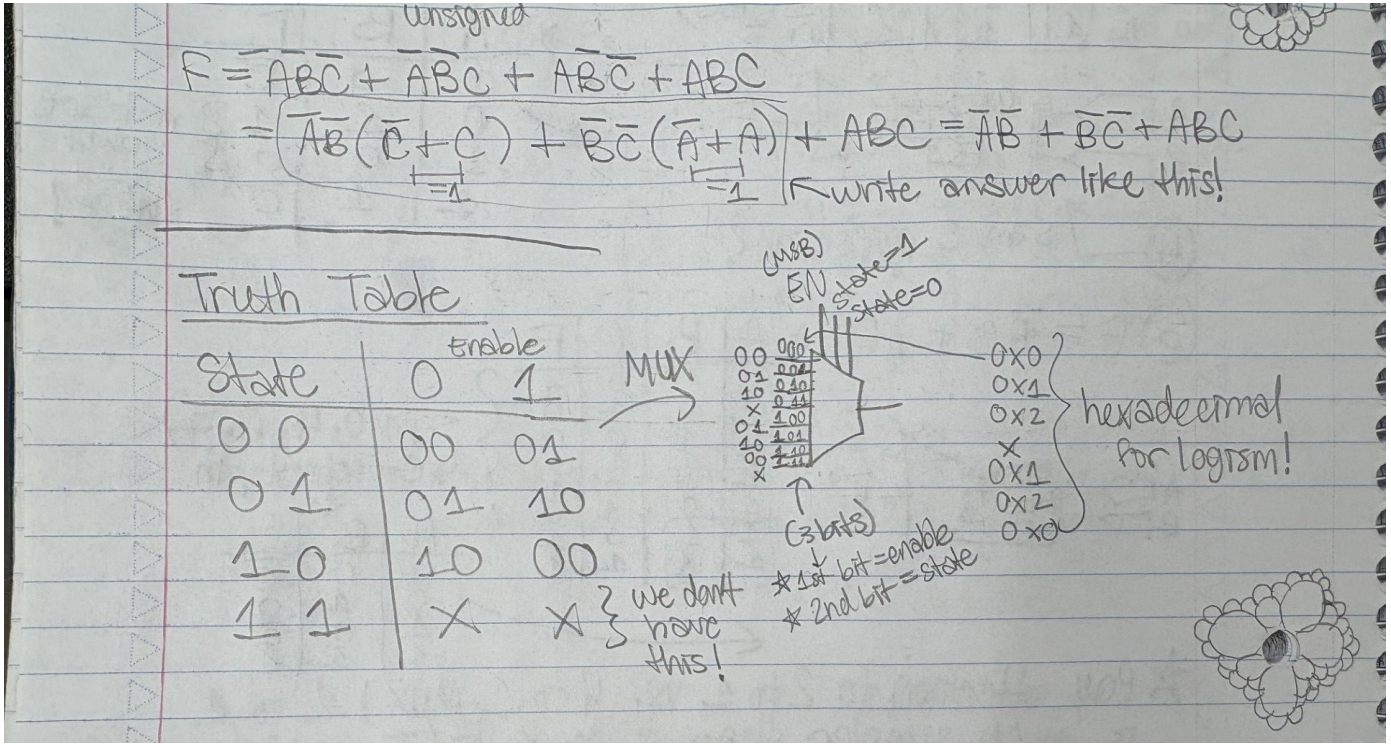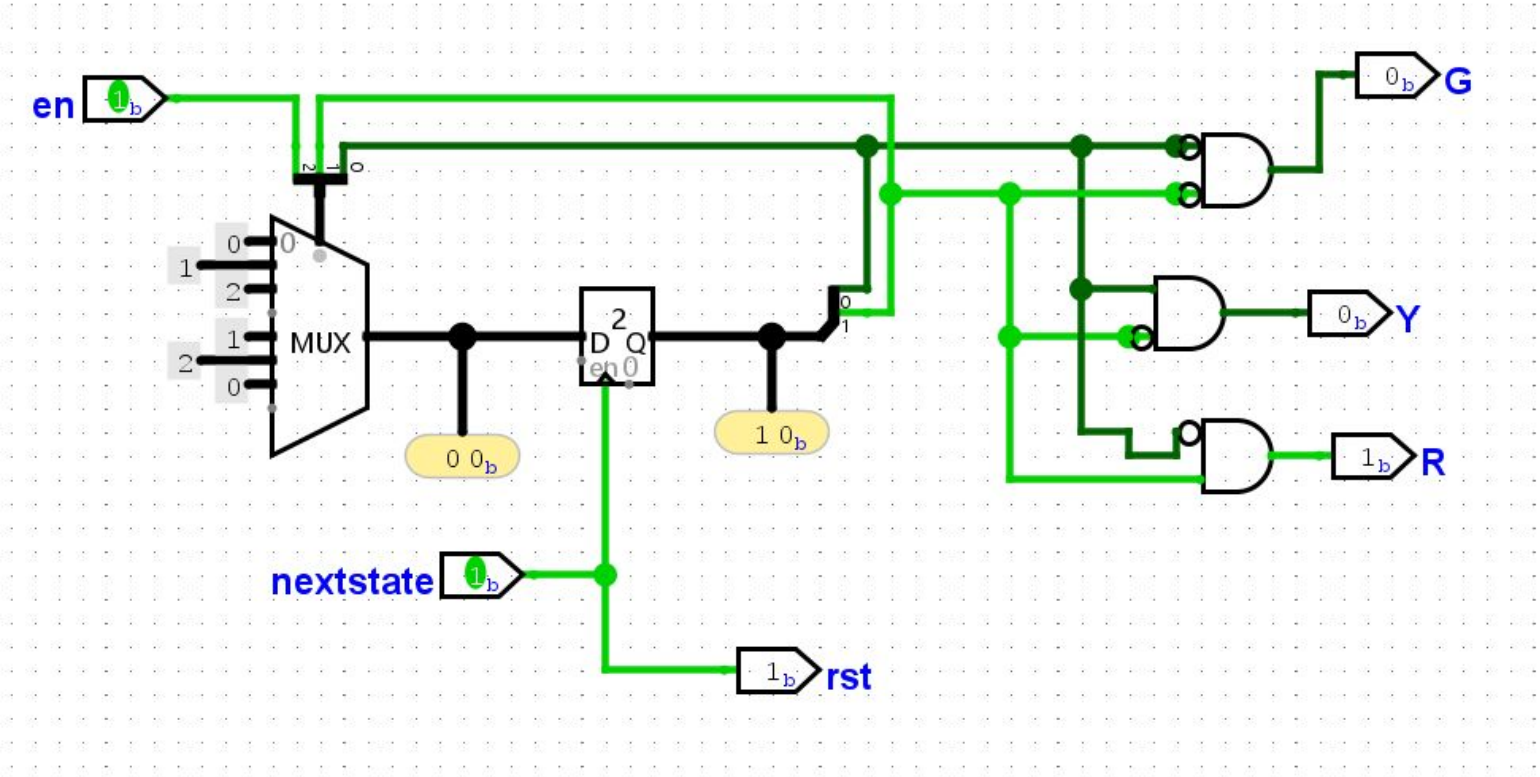

Truth table result with ands and nots



Final outcome (works!)

