Lab 8

Eden Aklilu

RGB rotation (8 states to cycle through)

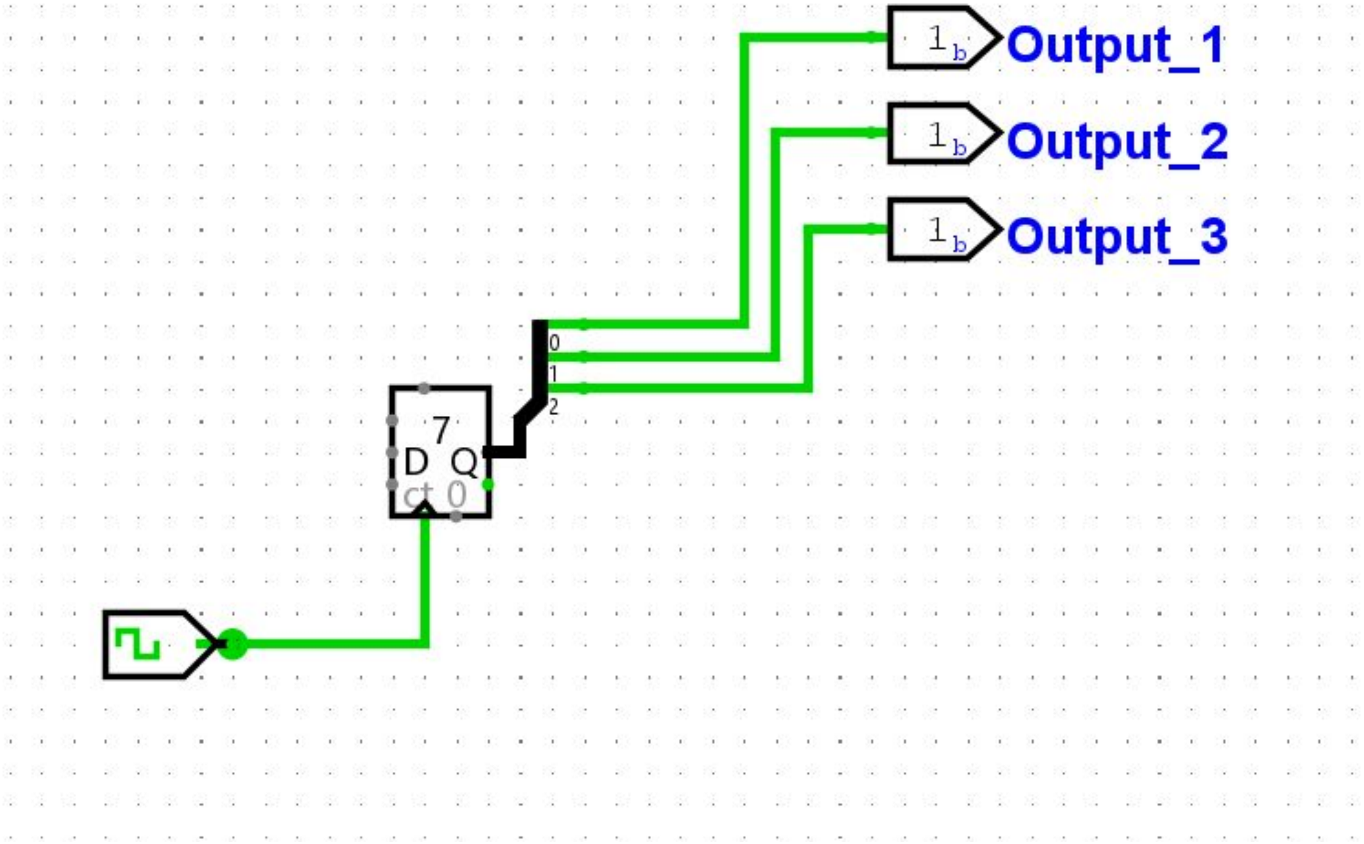

My attempts

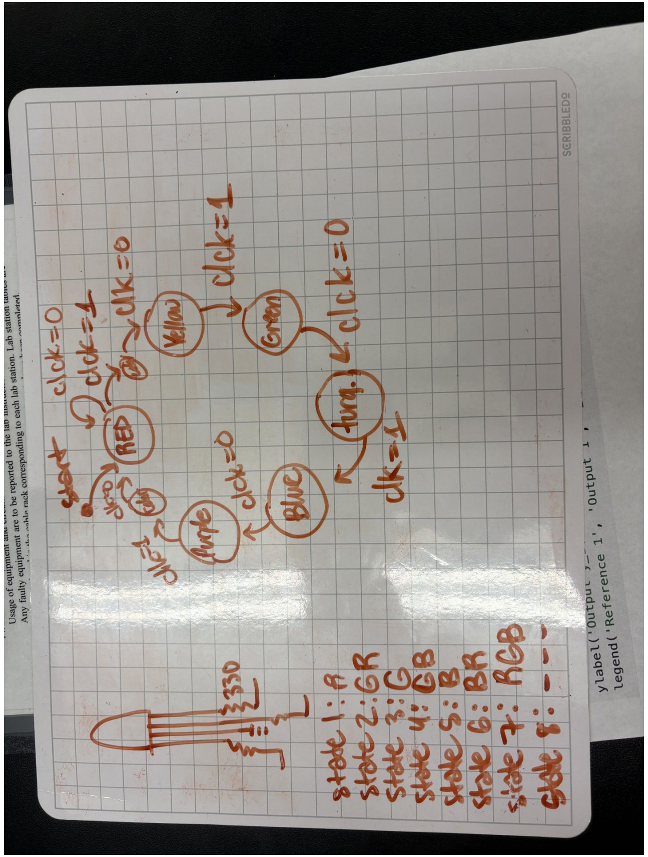

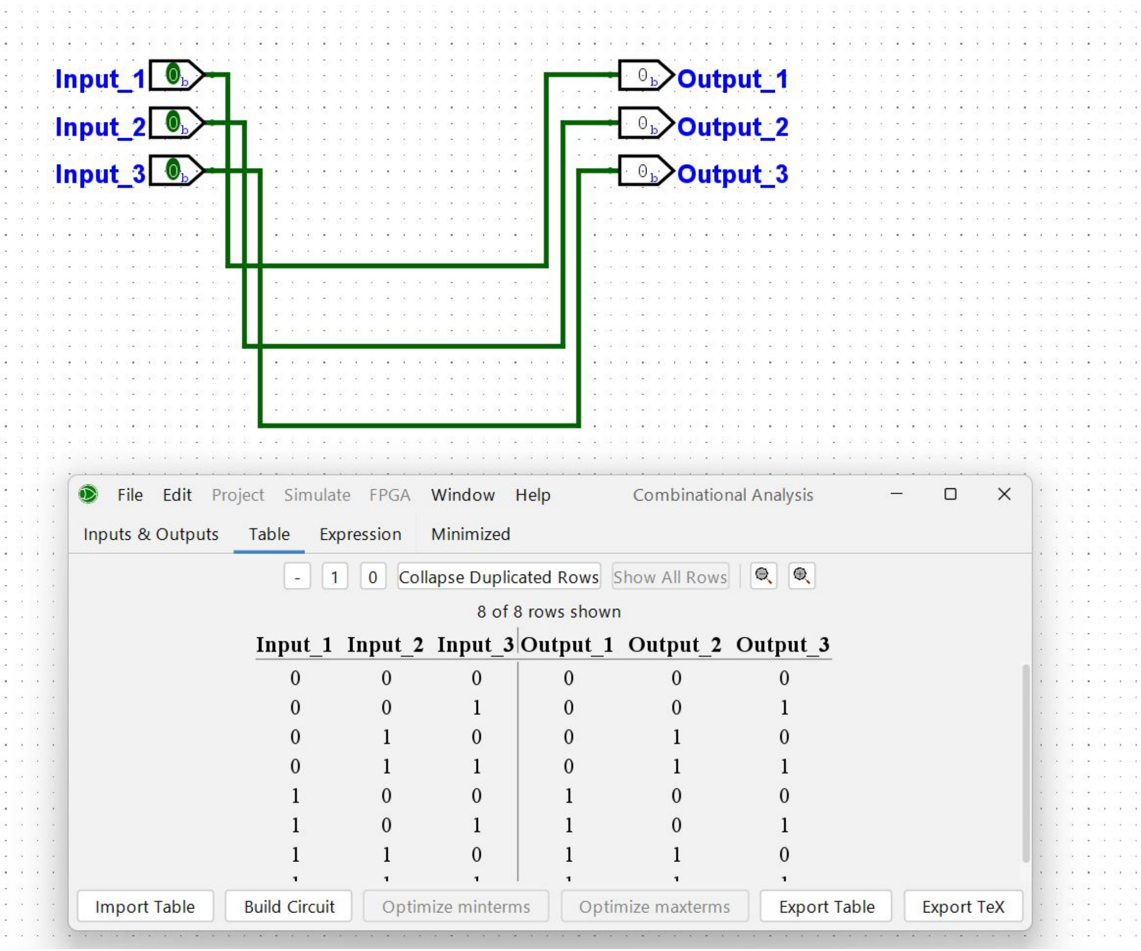

8 of 8 rows shown

Input_1	Input_2	Input_3	Output_1	Output_2	Output_3
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	0

Dr. Martins solution!! (top splitter used to extract red and green for extra states, mux used to decode the 3 inputs/scenarios)